California State University, Northridge

Department of Electrical & Computer Engineering




ECE 526L Lab 6 Report

By
Avinash Damse
CSUN ID- 203131064

 1: Introduction

The objective of this lab is to build Verilog model for a scalable multiplexer using behavioral Verilog and Familiarization with instance-by-instance parameter specification.

Here we have to use following diagram to build scalable multiplexer.



2: Procedure

a. Part 1: Creating mux Module

In this lab I have created a mux module for scalable multiplexer. Inside the module I have assigned "A, B and SEL," as input variables and "OUT" as output variables. Then I wrote the scalable multiplexter logic inside module. After completing the code I ended the module using and saved the file with name "mux.v".

b. Part 2: Creating mux_tb Module


I have written the test bench for the mux module. We require test bench just to make sure that the module we have created is working properly. Here, in this testbench I instantiated the mux module and wrote some test cases to check the output.

c. Part 3: execution.

Using "vcs -debug -full64 mux.v mux_tb.v" command I executed the file.

 d. Part 4: Simulation

After an execution of all modules, I have run the command "simv" for simulation.




```
ter N-2017.12-SP2-9_Full64 Copyright (c) 1991-2017 by Synopsys Inc.
      *********** SEL = 0 ***********
         0 A = 1010 B = 0011 SEL = 0 OUT1 = 0 OUT4 = 10 OUT5 = 010 OUT6 = 1010
         10 A = 1011 B = 0100 SEL = 0 OUT1 = 1 OUT4 = 11 OUT5 = 011 OUT6 = 1011
20 A = 1011 B = 1011 SEL = 0 OUT1 = 1 OUT4 = 11 OUT5 = 011 OUT6 = 1011
         30 A = 1011 B = 1011 SEL = 1 OUT1 = 1 OUT4 = 11 OUT5 = 011 OUT6 = 1011
         40 A = 1011 B = 0100 SEL = 1 OUT1 = 0 OUT4 = 00 OUT5 = 100 OUT6 = 0100
50 A = 1011 B = 1011 SEL = 1 OUT1 = 1 OUT4 = 11 OUT5 = 011 OUT6 = 1011
         60 A = 1011 B = 1011 SEL = x OUT1 = 1 OUT4 = 11 OUT5 = 011 OUT6 = 1011
         70 A = 1001 B = 0110 SEL = x OUT1 = x OUT4 = xx OUT5 = xxx OUT6 = xxxx
        ******* A = B ****************
         80 A = 1011 B = 1100 SEL = x OUT1 = x OUT4 = xx OUT5 = xxx OUT6 = 1xxx
        100 A = 1101 B = 1101 SEL = x OUT1 = 1 OUT4 = 01 OUT5 = 101 OUT6 = 1101
        110 A = 1001 B = 1001 SEL = x OUT1 = 1 OUT4 = 01 OUT5 = 001 OUT6 = 1001
called from file "mux_tb.v", line 60.
at simulation time
                               120
         Simulation
                            Report
```

e. Part 5: Creating Log File

After running the simulation I created the log file using the "simv -I Lab6.log" command.

 f. Part 6: Seeing the waveform.

After creating the log file I opened the DVE using "dve -full64 &" command to see the waveforms.



Conclusion:

The functionality of the scalable multiplexer coded in this lab was successfully verified. In addition to the normal features of a multiplexer, it has the capability to resolve conflicting bits upon setting SEL to x. The instances were also successfully created with the parameters modified according to specification.

I hereby attest that this lab report is entirely my own work. I have not copied either code or text from anyone, nor have I allowed or will I allow anyone to copy my work.

Name (printed) Avinash Damse

Name(signed)



Date: 5-April-2023